

Part I:

5

1. $R_A = \underline{2.4 \Omega} \quad \frac{1}{2}$

1

$R_B = \underline{1.7 \Omega} \quad \frac{1}{2}$


2.





5


3. $\alpha(f) = (a \pm \Delta a) \text{ mm}^{-1} + (b \pm \Delta b) \frac{\text{mm}^{-1}}{\text{kHz}} f$

1

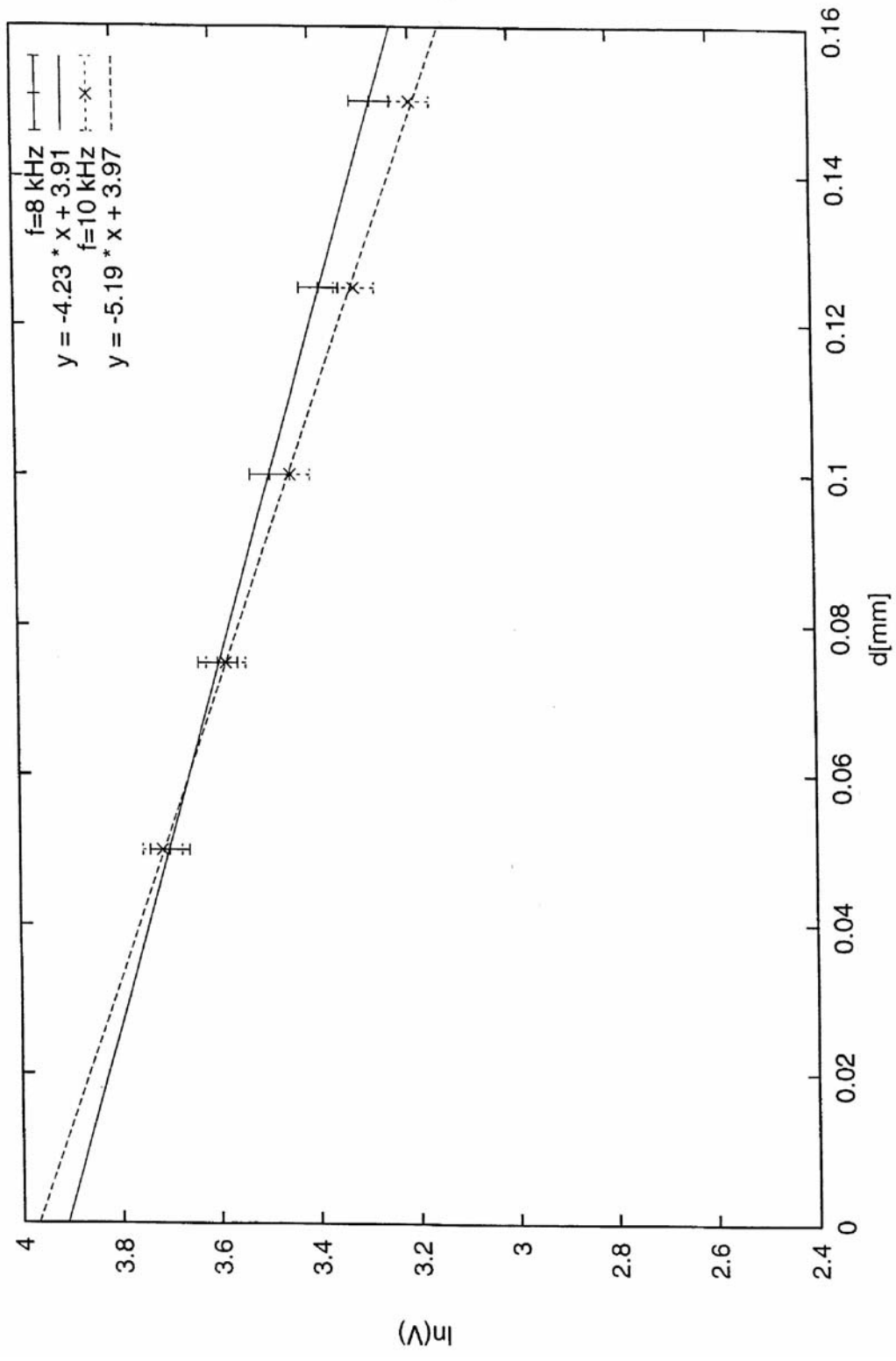

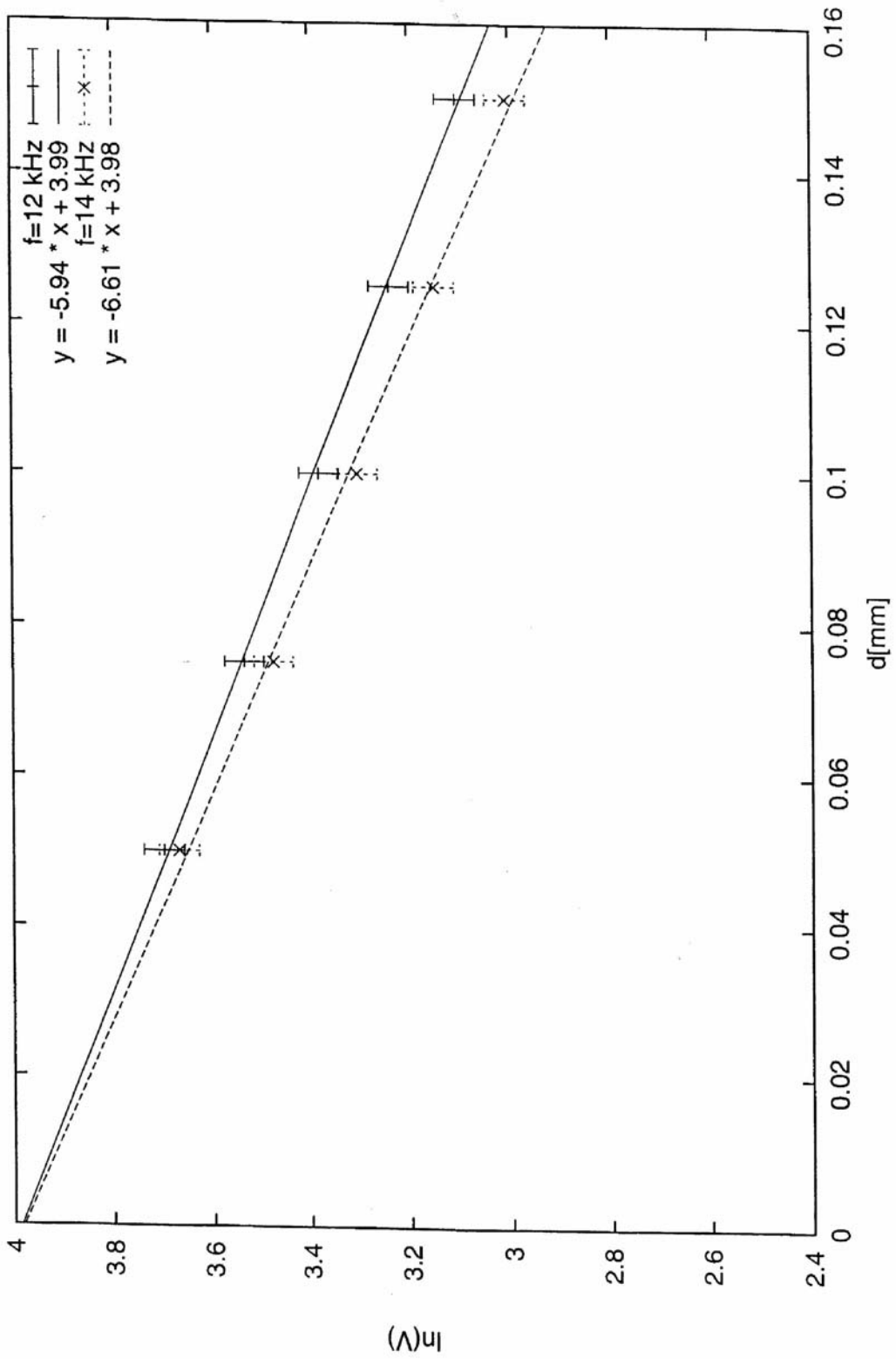

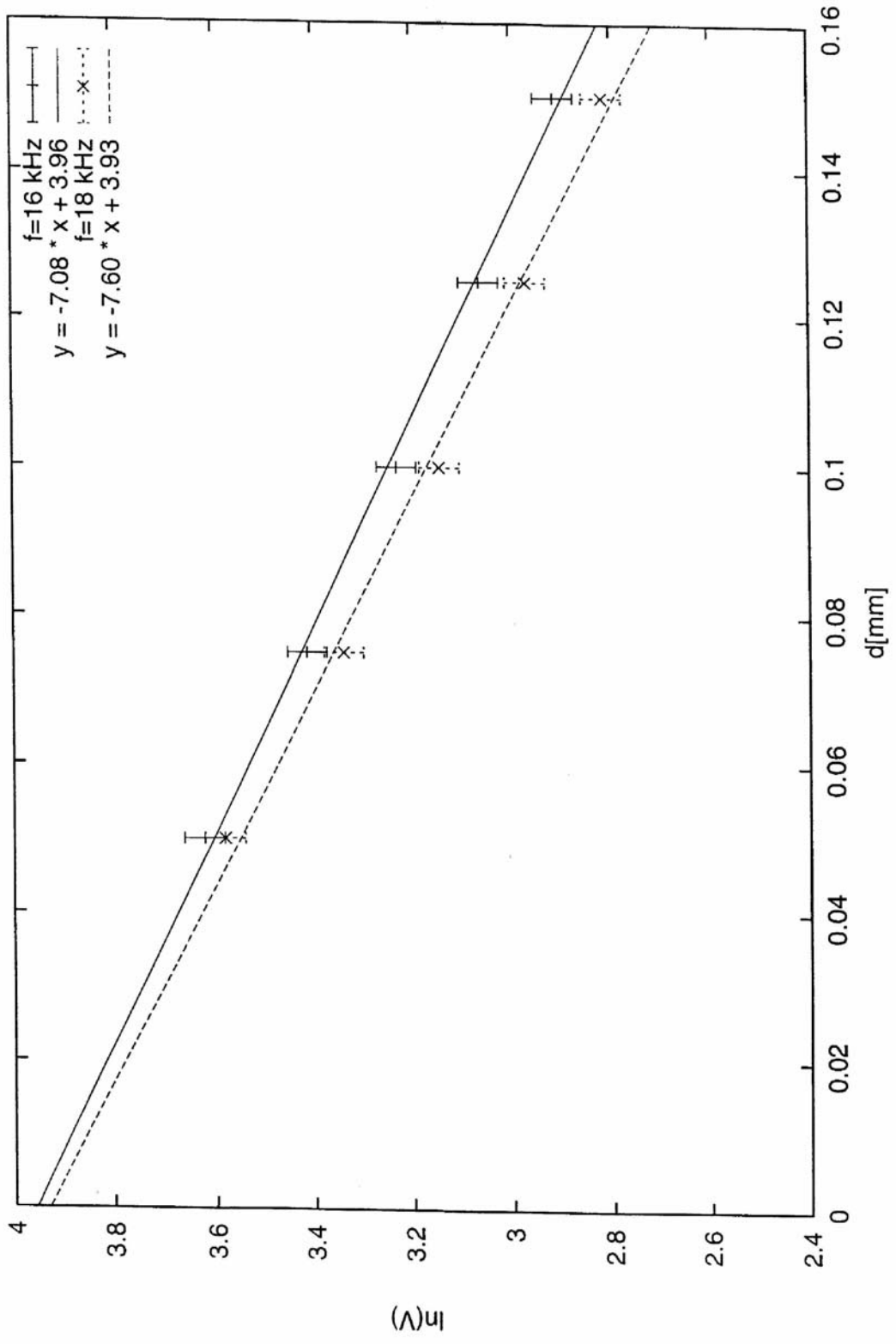

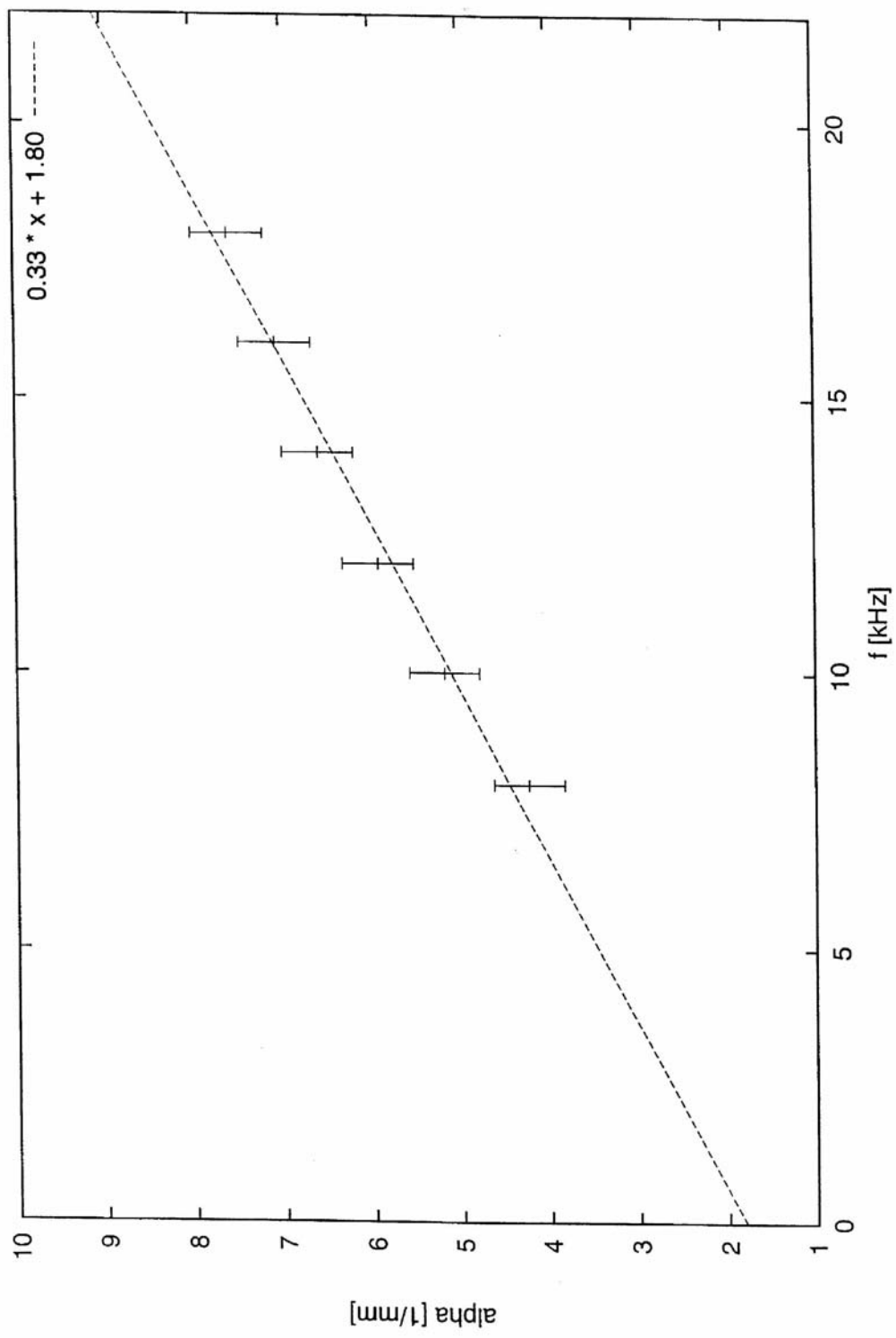


Part II: (1?)

1.a. $L_A = \frac{\varepsilon_A}{\omega I_A^2}$, $I_B = 0$ (1/2)

$L_B = \frac{\varepsilon_B}{\omega I_B^2}$, $I_A = 0$ (1/3)

$k = \frac{N_A}{N_B} \frac{\varepsilon_B}{\varepsilon_A}$, $I_B = 0$ | $k = \frac{N_B}{N_A} \frac{I_B}{I_A}$, $V_B = 0$ (1/3)

1.b.

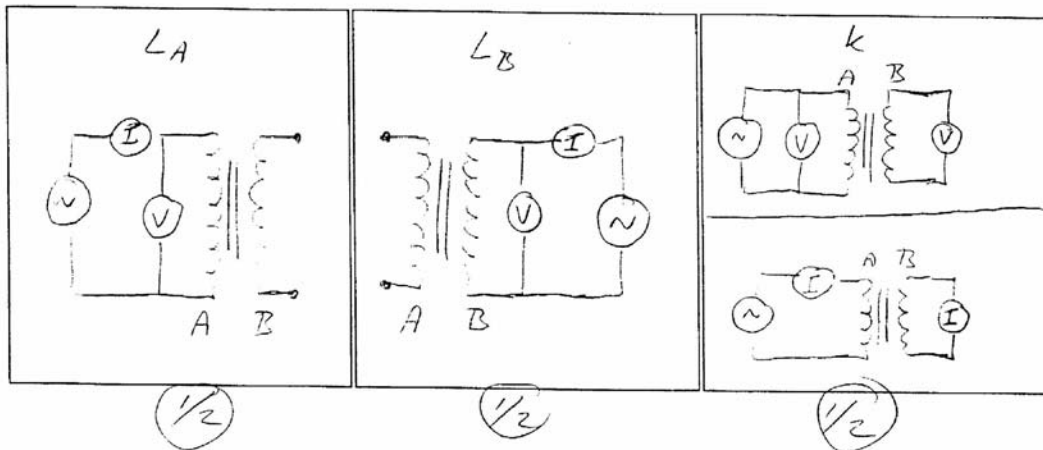

1.c. $L_A = \underline{34 \pm 3 \text{ mH}}$ (1/3)

$L_B = \underline{15 + 1 \text{ mH}}$ (1/3)

$k = \underline{\quad \quad \quad}$ (1/3)

$$2.a. I_p = \frac{\epsilon_A}{\omega L_A (1 - k^2)}, \quad V_B = 0 \quad \underline{1}$$

$$2.b. I_p = \underline{66 \pm 3 \text{ mA}} \quad \underline{1}$$

$$3.1. L_{A+B} = \underline{95 \pm 6 \text{ mH}} \quad \underline{1/2}$$

$$3.2.a. V_A = \underline{16.0 \pm 0.6 \text{ V}} \quad \underline{1/2}$$

$$V_B = \underline{8.4 \pm 0.3 \text{ V}} \quad \underline{1/2}$$

$$3.2.b. \frac{V_A}{V_B} = \underline{1.91 \pm 0.12} \quad \underline{1/2}$$

$$3.2.c. \frac{V_A}{V_B} = \frac{N_A^2 - k M_A N_B}{N_B^2 - k M_B N_A} \quad \underline{1/2}$$

$$4. \quad \frac{L}{N^2} = C$$

$$\frac{L_A}{N_A^2} = 1.5 \cdot 10^{-6} \text{ H}$$

$$\frac{L_B}{N_B^2} = 1.5 \cdot 10^{-6} \text{ H}$$

$$\frac{L_{A+B}}{(N_A+N_B)^2} = 1.5 \cdot 10^{-6} \text{ H} \quad \left(\frac{1}{2}\right)$$

$$5. \quad R_H = 2.4 \Omega \ll (N L_{11})_{\min} (1-k^2) = 100 \Omega$$

$$6.a. \quad \mu_r = \frac{l_f}{d} \left(\frac{V_1}{Z_1} \frac{L_2}{V_2} - 1 \right) = \frac{l_f}{d} \left(\frac{L_1}{L_2} - 1 \right) \quad (1)$$

$$6.b. \quad \mu_r = \underline{2300} \approx 400 \quad (1)$$

Part II

1. A primary B secondary $f = 10 \text{ kHz}$

$$L_A = \frac{\epsilon_A}{\omega I_A}, \quad I_B = 0$$

B primary A secondary

$$L_B = \frac{\epsilon_B}{\omega I_B}, \quad I_A = 0$$

A primary B secondary
Secondary open $I_B = 0$

$$\left. \begin{aligned} \epsilon_A &= c \omega N_A^2 I_A \\ \epsilon_B &= c \omega k N_A N_B I_A \end{aligned} \right\} k = \frac{N_A \epsilon_B}{N_B \epsilon_A}$$

or

secondary closed $\epsilon_B = 0$

$$\epsilon_B = c \omega N_B (N_B I_B - k N_A I_A) = 0$$

$$\Rightarrow k = \frac{N_B I_B}{N_A I_A}$$

Part II

2. A primary B secondary $f = 10 \text{ kHz}$

Open secondary $\varepsilon_A = c \omega N_A^2 I_A = \omega L_A I_A$

$$\Rightarrow L_A = c N_A^2$$

Closed secondary

$$\varepsilon_A = c \omega N_A (N_A I_A - k N_B I_B)$$

$$\varepsilon_B = c \omega N_B (N_B I_B - k N_A I_A) = 0$$

$$\Rightarrow I_B = k \frac{N_A}{N_B} I_A$$

$$\Rightarrow \varepsilon_A = \omega c N_A^2 (1 - k^2) I_A = \omega L_A (1 - k^2) I_A$$

$$\underline{\underline{I_D = I_A = \frac{\varepsilon_A}{\omega L_A (1 - k^2)}}}$$

Past II

3.2.c Flux subtraction

$$I = I_A = I_B$$

$$V_A = \mathcal{E}_A = \omega c N_A I (N_A - k N_B)$$

$$V_B = \mathcal{E}_B = \omega c N_B I (N_B - k N_A)$$

$$\frac{V_A}{V_B} = \frac{N_A^2 - k N_A N_B}{N_B^2 - k N_A N_B}$$

Past II


$$4. \quad L = c N^2 \quad \frac{L}{N^2} = c \text{ constant}$$

$$5. \quad R_A = 2.4 \Omega \ll (\omega L_A)_{\min} (1 - k^2) \approx 100 \Omega$$

6. Closed magnetic circuit

$$N I_1 = \oint \frac{1}{\mu_f} \vec{B} \cdot d\vec{l} = \frac{2l_f}{\mu_f} B_1$$

$$V_1 = N \dot{\Phi} = \omega N B_1 A$$

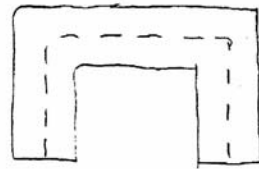

l_f length of
central dotted
line

Paper gap circuit

$$N I_2 = \oint \frac{1}{\mu} \vec{B} \cdot d\vec{l} = \left(\frac{2l_f}{\mu_f} \pm \frac{2d}{\mu_0} \right) B_2$$

$$V_2 = N \dot{\Phi}_2 = \omega N B_2 A$$

$$\frac{I_2 B_1}{B_2 I_1} = 1 + \frac{d}{l_f} \frac{\mu_f}{\mu_0}$$

$$\begin{aligned} \mu_r = \frac{\mu_f}{\mu_0} &= \left(\frac{I_2 B_1}{B_2 I_1} - 1 \right) \frac{l_f}{d} = \frac{l_f}{d} \left(\frac{I_2}{V_2} \frac{V_1}{I_1} - 1 \right) \\ &= \frac{l_f}{d} \left(\frac{L_1}{L_2} - 1 \right) \end{aligned}$$